


EE 577A- Fall 2021 VLSI SYSTEM DESIGN

Lab2 Report
512-bit SRAM Array Design

Ti-Shen Chueh
tchueh@usc.edu

3751474091

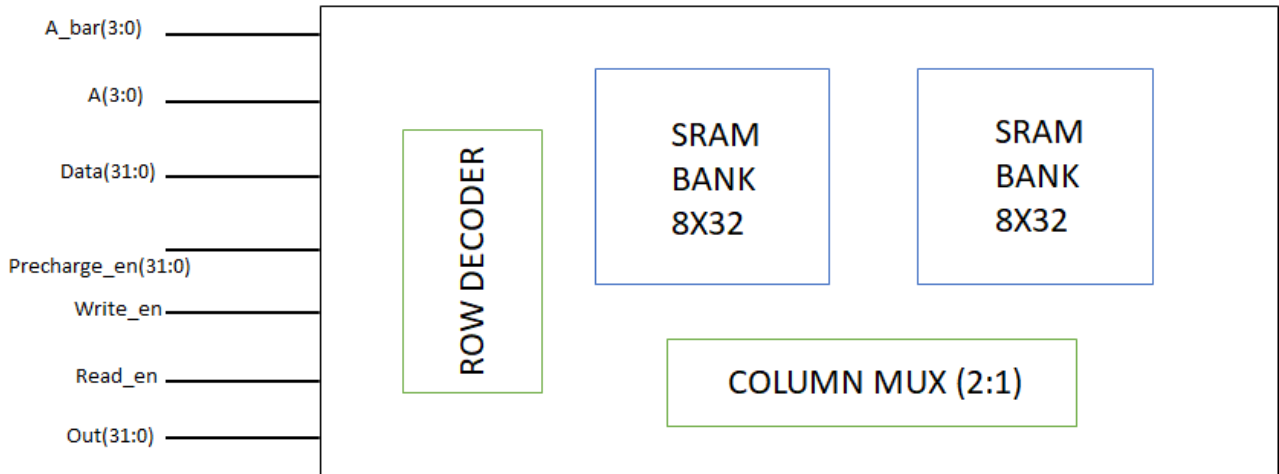
In this lab, we will design a 512-bit SRAM with two 256-bit banks. The word length is 16 bits.




Below is the summary of the input pins:

INPUT	ADDRESS BITS	$A[3]-A[0], A_{\text{bar}}[3]-A_{\text{bar}}[0]$	Transition time =5ps
INPUT	READ CONTROL	<u>Read_en</u>	Transition time =5ps
INPUT	WRITE CONTROL	<u>Write_en</u>	Transition time =5ps
INPUT	PRECHARGE CONTROL	<u>Precharge_en</u>	Transition time =5ps
INPUT	WRITE DATA BITS	$\text{Data}[31]-\text{data}[0]$	Transition time =5ps
INPUT	READ DATA BITS	$\text{Out}[31]-\text{out}[0]$	Transition time =5ps


3-8 Decoder (Schematic)

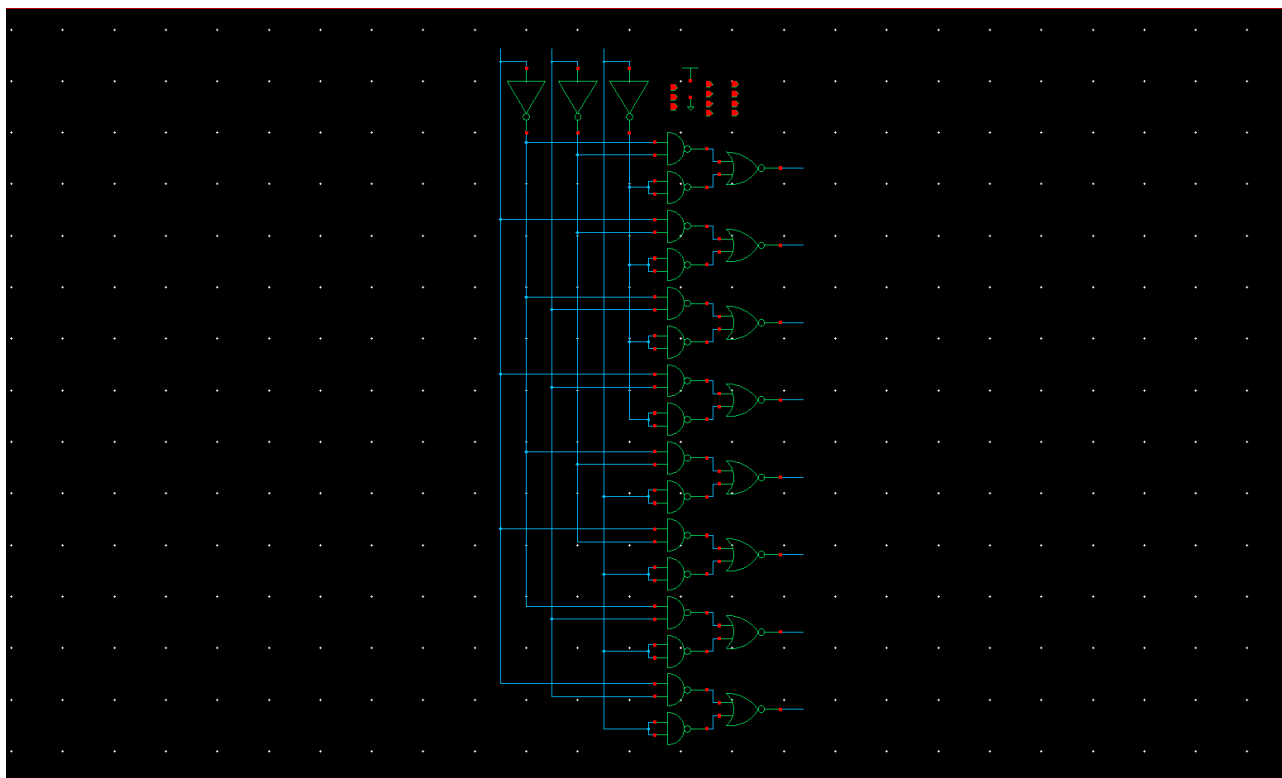

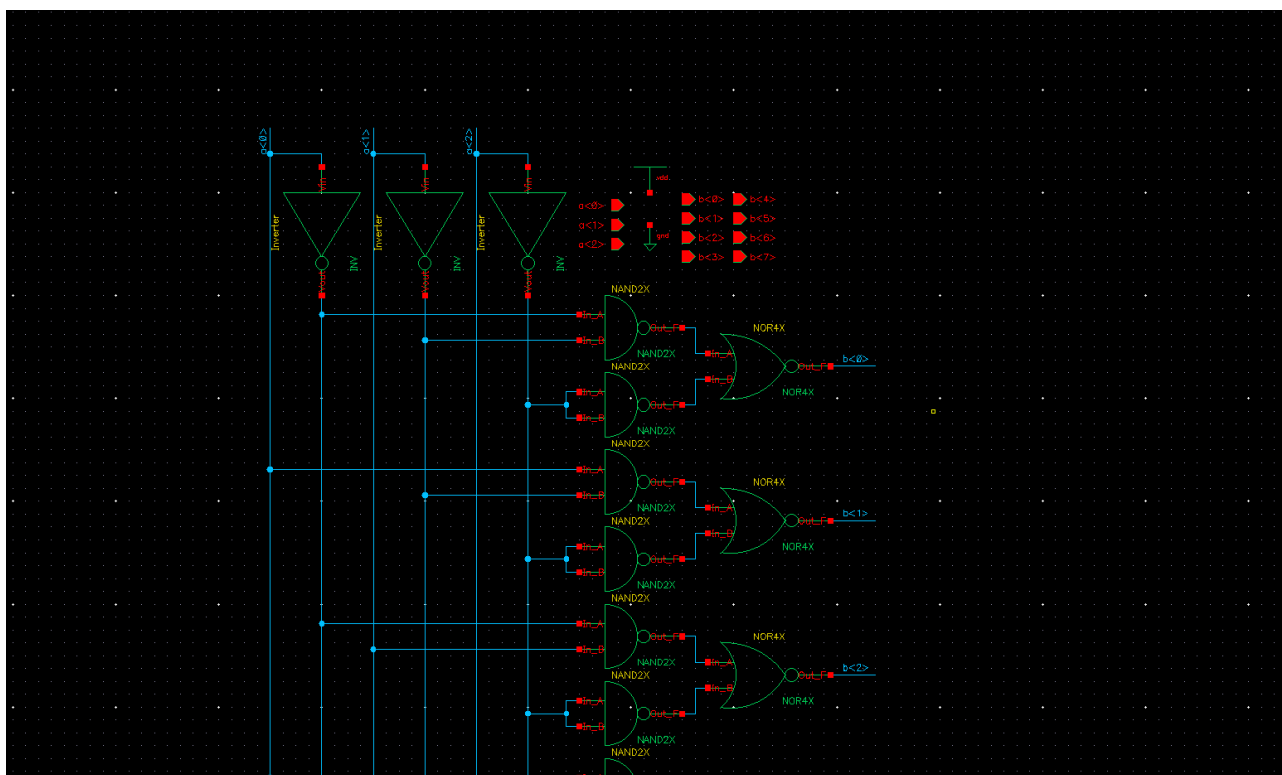The figure below is the pre-decode system for 3-8 decoder.



3-8 Decoder (Layout)

 

PVS 16.15-64b Reports: Done [DRC] DR...

[DRC] DRC x

```
DRG: Cumulative Time CPU = 0 (s) REAL = 0 (s)
PATTERN_MATCH: Cumulative Time CPU = 0 (s) REAL = 0 (s)
DFM FILL: Cumulative Time CPU = 0 (s) REAL = 0 (s)

Total CPU Time : 1 (s)
Total Real Time : 1 (s)
Peak Memory Used : 30 (M)
Total Original Geometry : 264 (3101)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file Decoder3_8.sum
ASCII
Check
```

PVS 16.15-64b DRC Results Viewer

File View Options Tools Windows Help

cadence

Fit and Zoom 0.40 Pan

Lab1::Decoder3_8:layout

Cell/Rule Hier Top Cells Rules Show: [Green] [Yellow] [Red] [Hand] [Cross] [Warning] [Info]

Explain Return On Top

Cell/Rule	Color	Count	Level
-----------	-------	-------	-------


Total: 0 results in 0 of 562 checks. Total number of non-empty checks is 0.

Find


Error

Help


/home/vite

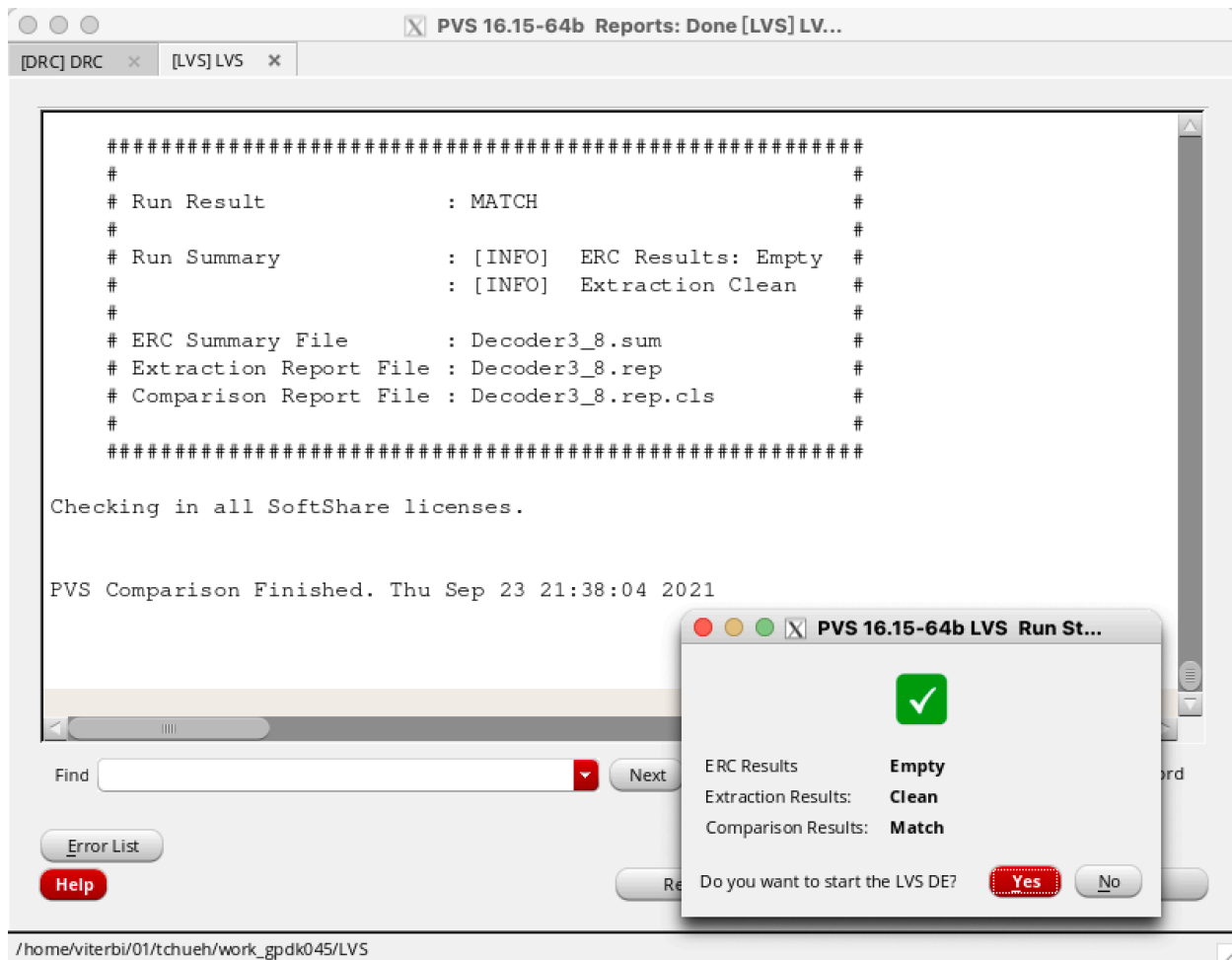

SRAM Cell (Schematic)

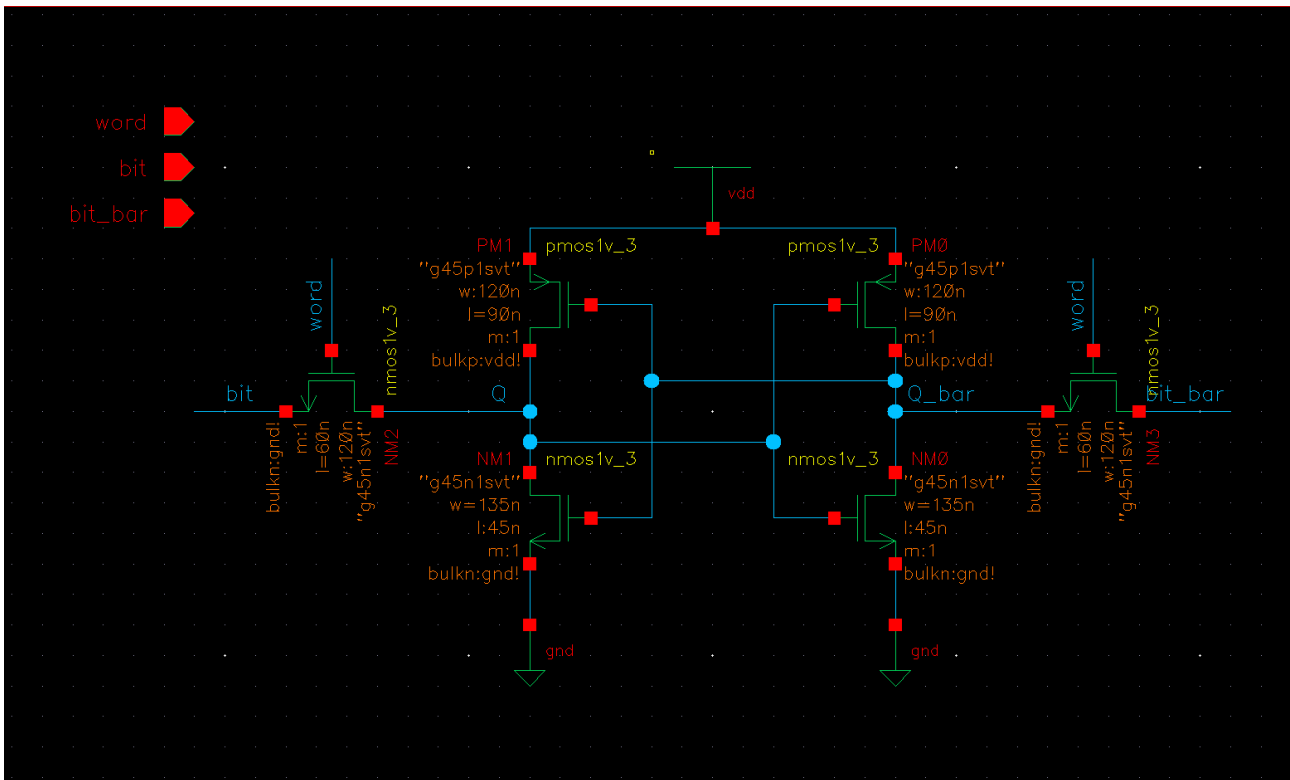

SRAM Cell (Layout)

 

PVS 16.15-64b Reports: Done [DRC] DR...

[LVS] LVS x [DRC] DRC x

```
ERC: Cumulative Time CPU = 0 (s) REAL = 0 (s)
PATTERN_MATCH: Cumulative Time CPU = 0 (s) REAL = 0 (s)
DFM FILL: Cumulative Time CPU = 0 (s) REAL = 0 (s)

Total CPU Time : 1 (s)
Total Real Time : 1 (s)
Peak Memory Used : 26 (M)
Total Original Geometry : 123 (193)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file SRAMCell.sum
ASCII re
Checking
```

PVS 16.15-64b DRC Results Viewer


File View Options Tools Windows Help

Lab1::PrechargeCell::layout x Lab1::SRAMCell::layout x


Cell/Rule	Color	Count	Level
-----------	-------	-------	-------

Total: 0 results in 0 of 562 checks. Total number of non-empty checks is 0.


/home/viterbi/01

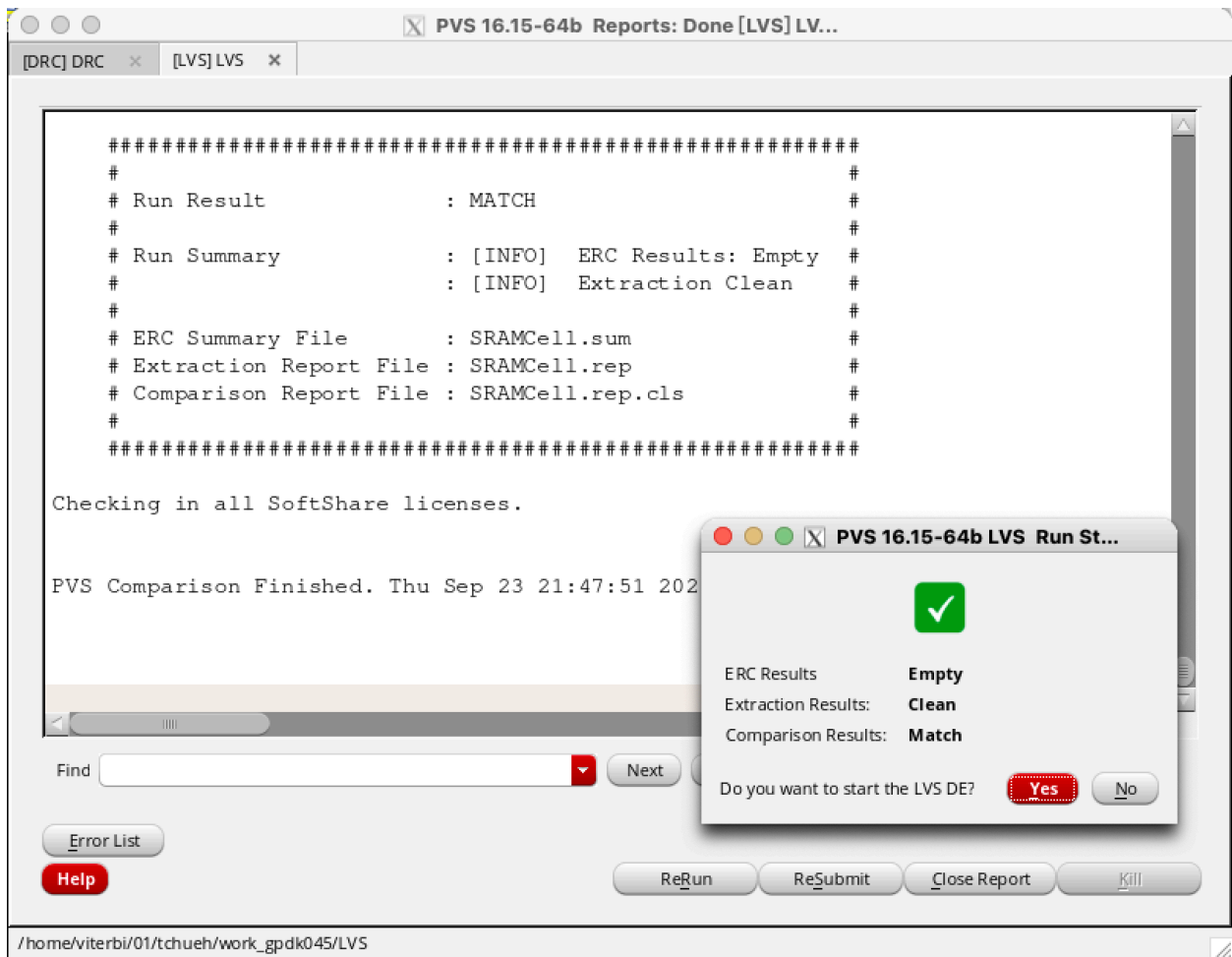


Write/Read MUX (Schematic)

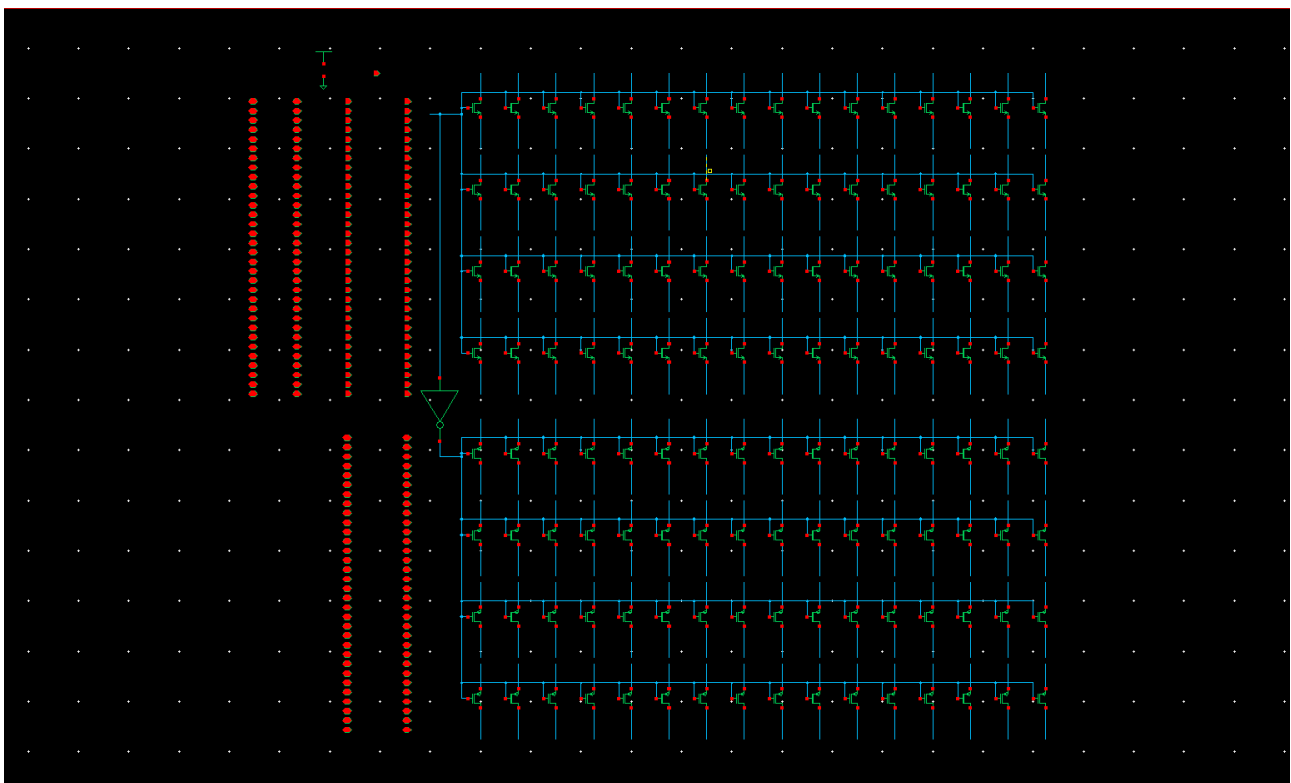


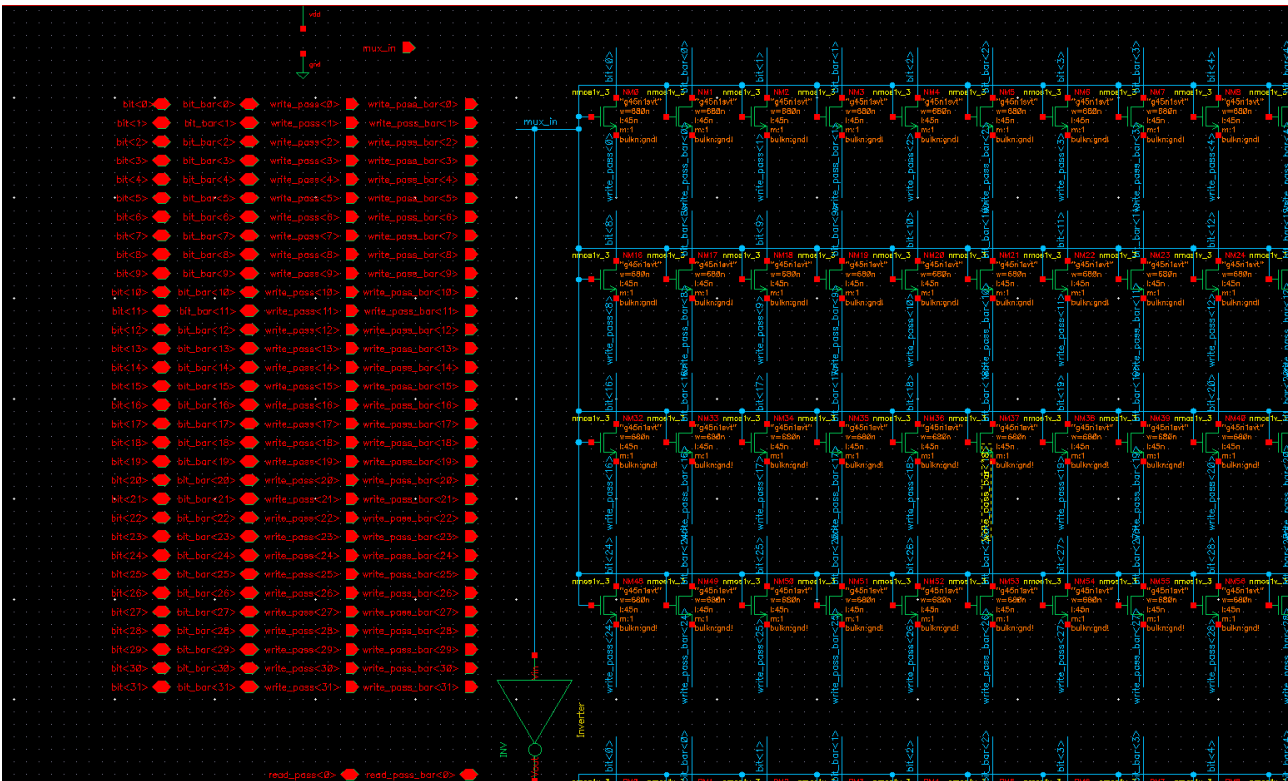
The figure below shows that nMOS pass transistors ($W = 680\text{nm} / L = 45\text{nm}$) is used to design the column write MUX.



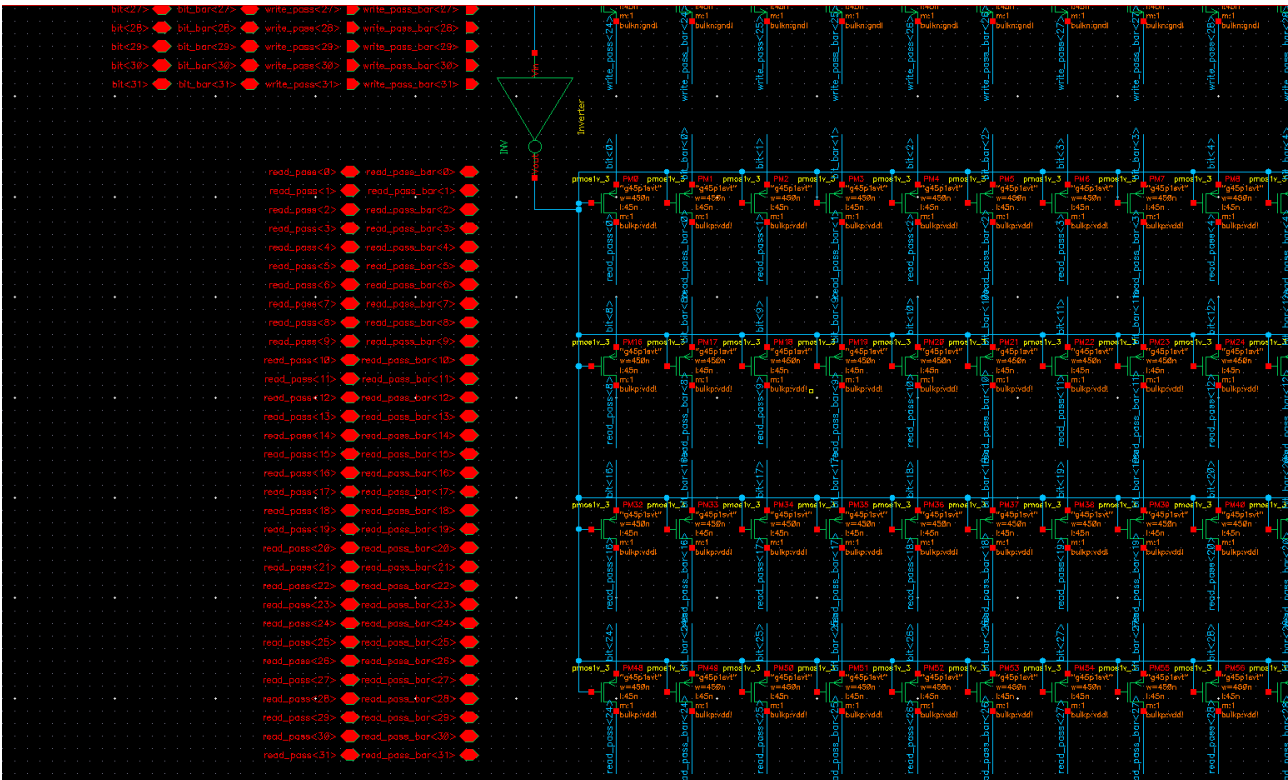The figure below shows that pMOS pass transistors ($W = 450\text{nm} / L = 45\text{nm}$) is used to design the column read MUX.



Write/Read MUX (Layout)

  

PVS 16.15-64b Reports: Done [DRC] DR...

[LVS] LVS x [DRC] DRC x

```

ERC: Cumulative Time CPU = 0 (s) REAL = 0 (s)
PATTERN_MATCH: Cumulative Time CPU = 0 (s) REAL = 0 (s)
DFM FILL: Cumulative Time CPU = 0 (s) REAL = 0 (s)

Total CPU Time : 1 (s)
Total Real Time : 2 (s)
Peak Memory Used : 34 (M)
Total Original Geometry : 885 (4104)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file MUX.sum
ASCII report database: /home/viterbi/01/tchueh/work_gpdk045/DRC/MUX
Checking

```

Design Rule

Lab1::MUX::layout

Cell/Rule Hier Top Cells Rules Show:

Explain Return On Top

Cell/Rule	Color	Count	Level
Total: 0 results in 0 of 562 checks. Total number of non-empty checks is 0.			

Find

Error List

Help

/home/viterbi/01/tchueh/work_gpdk045/LVS

PVS 16.15-64b Reports: Done [LVS] LV...

[DRC] DRC x [LVS] LVS x

```

#####
#
# Run Result : MATCH #
#
# Run Summary : [INFO] ERC Results: Empty #
# : [INFO] Extraction Clean #
# : [INFO] Some Sections Have Been Truncated #
#
# ERC Summary File : MUX.sum #
# Extraction Report File : MUX.rep #
# Comparison Report File : MUX.rep.cls #
#
#####

```

Checking in all SoftShare licenses.

PVS Comparison Finished. Thu Sep 23 22:12:39 202

Find

Error List

Help

ReRun ReSubmit Close Report Kill

PVS 16.15-64b LVS Run St...

ERC Results: **Empty**

Extraction Results: **Clean**

Comparison Results: **Match**

Do you want to start the LVS DE? **Yes** No

/home/viterbi/01/tchueh/work_gpdk045/LVS

PVS 16.15-64b Reports: Done [DRC] DR...

[LVS] LVS x [DRC] DRC x

```

ERC: Cumulative Time CPU = 0 (s) REAL = 0 (s)
PATTERN_MATCH: Cumulative Time CPU = 0 (s) REAL = 0 (s)
DFM FILL: Cumulative Time CPU = 0 (s) REAL = 0 (s)

Total CPU Time : 1 (s)
Total Real Time : 1 (s)
Peak Memory Used : 26 (M)
Total Original Geometry : 93 (202)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file PrechargeCell.sum

```

ASCII

Check

Design

Find

Error

Help

PVS 16.15-64b DRC Results Viewer

File View Options Tools Windows Help

cadence

Lab1:PrechargeCell:layout

Cell/Rule Hier Top Cells Rules Show: [Icons]

Navigator

Cell/Rule	Color	Count	Level
Total: 0 results in 0 of 562 checks. Total number of non-empty checks is 0.			

/home/viterbi

PVS 16.15-64b Reports: Done [LVS] LV...

[DRC] DRC x [LVS] LVS x

```

#####
#
# Run Result : MATCH #
#
# Run Summary : [INFO] ERC Results: Empty #
# : [INFO] Extraction Clean #
#
# ERC Summary File : PrechargeCell.sum #
# Extraction Report File : PrechargeCell.rep #
# Comparison Report File : PrechargeCell.rep.cls #
#
#####

```

Checking in all SoftShare licenses.


PVS Comparison Finished. Thu Sep 23 21:44:20 2021

Find

Error List

Help

PVS 16.15-64b LVS Run St...



ERC Results **Empty**


Extraction Results: **Clean**

Comparison Results: **Match**


Do you want to start the LVS DE? **Yes** No

ReRun ReSubmit Close Report Kill

Sense Amp. (Schematic)

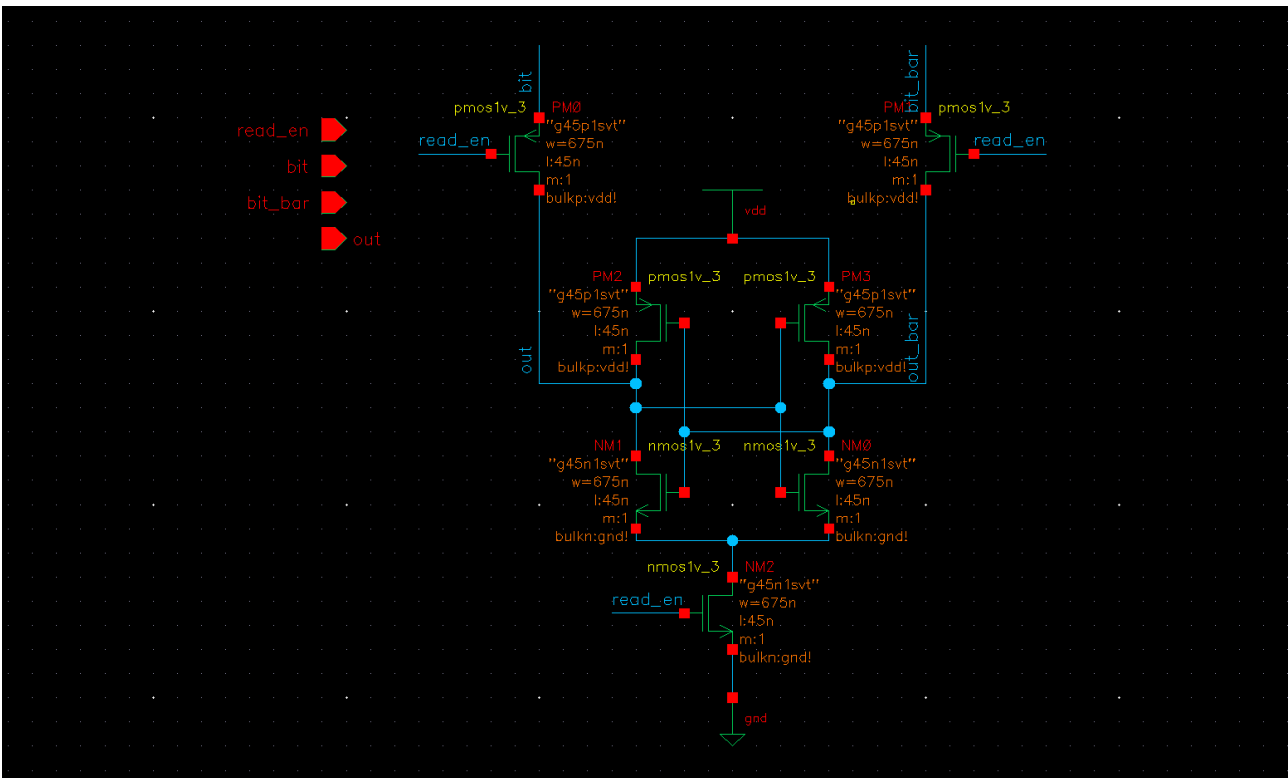

Sense Amp. (Layout)

 

PVS 16.15-64b Reports: Done [DRC] DR...

[LVS] LVS x [DRC] DRC x

```

    ERC: Cumulative Time CPU =      0 (s) REAL =      0 (s)
  PATTERN_MATCH: Cumulative Time CPU =      0 (s) REAL =      0 (s)
    DFM FILL: Cumulative Time CPU =      0 (s) REAL =      0 (s)

Total CPU Time           : 1 (s)
Total Real Time          : 1 (s)
Peak Memory Used         : 26 (M)
Total Original Geometry  : 168 (349)
Total DRC RuleChecks     : 562
Total DRC Results        : 0 (0)
Summary can be found in file SenseAmpCell.sum
ASCII re
Checking
Design E

```

PVS 16.15-64b DRC Results Viewer

File View Options Tools Windows Help

cadence

Lab1::PrechargeCell::layout x Lab1::SRAMCell::layout x Lab1::SenseAmpCell::layout x

Cell/Rule Hier Top Cells Rules Show: [check] [warn] [error] [info]

Cell/Rule	Color	Count	Level
Total: 0 results in 0 of 562 checks. Total number of non-empty checks is 0.			

Find

Error List

Help

/home/viterbi/01

PVS 16.15-64b Reports: Done [LVS] LV...

[DRC] DRC x [LVS] LVS x

```

#####
#
# Run Result           : MATCH
#
# Run Summary          : [INFO] ERC Results: Empty
#                      : [INFO] Extraction Clean
#
# ERC Summary File     : SenseAmpCell.sum
# Extraction Report File : SenseAmpCell.rep
# Comparison Report File : SenseAmpCell.rep.cls
#
#####
Checking in all SoftShare licenses.

PVS Comparison Finished. Thu Sep 23 21:51:45 2021

```

Find


Error List

Help

ReRun ReSubmit Close Report Kill

/home/viterbi/01/tchueh/work_gpdk045/LVS

PVS 16.15-64b LVS Run St...




ERC Results: **Empty**

Extraction Results: **Clean**


Comparison Results: **Match**

Do you want to start the LVS DE? **Yes** No


Register (Schematic)

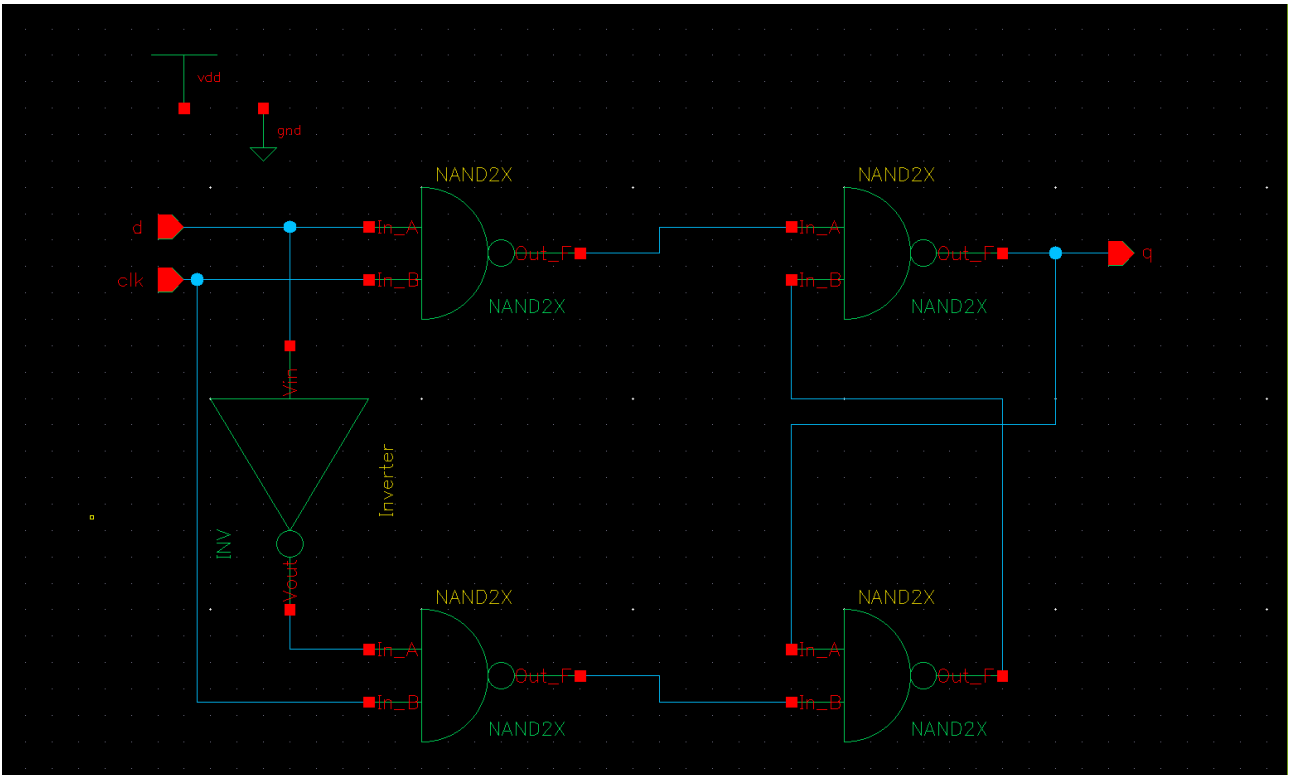


Register (Layout)

 


Write Path (Schematic)

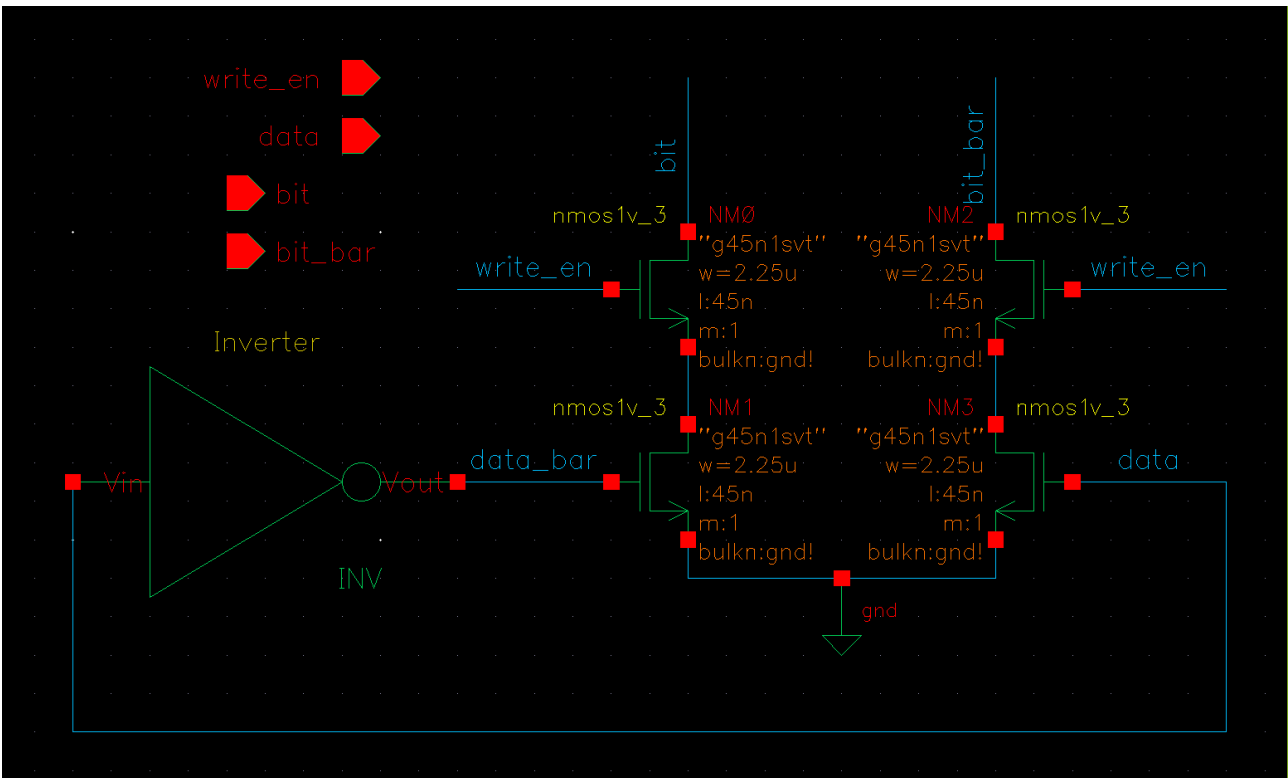


Write Path (Layout)

 


SRAM 8x32 Bank (Schematic)

 

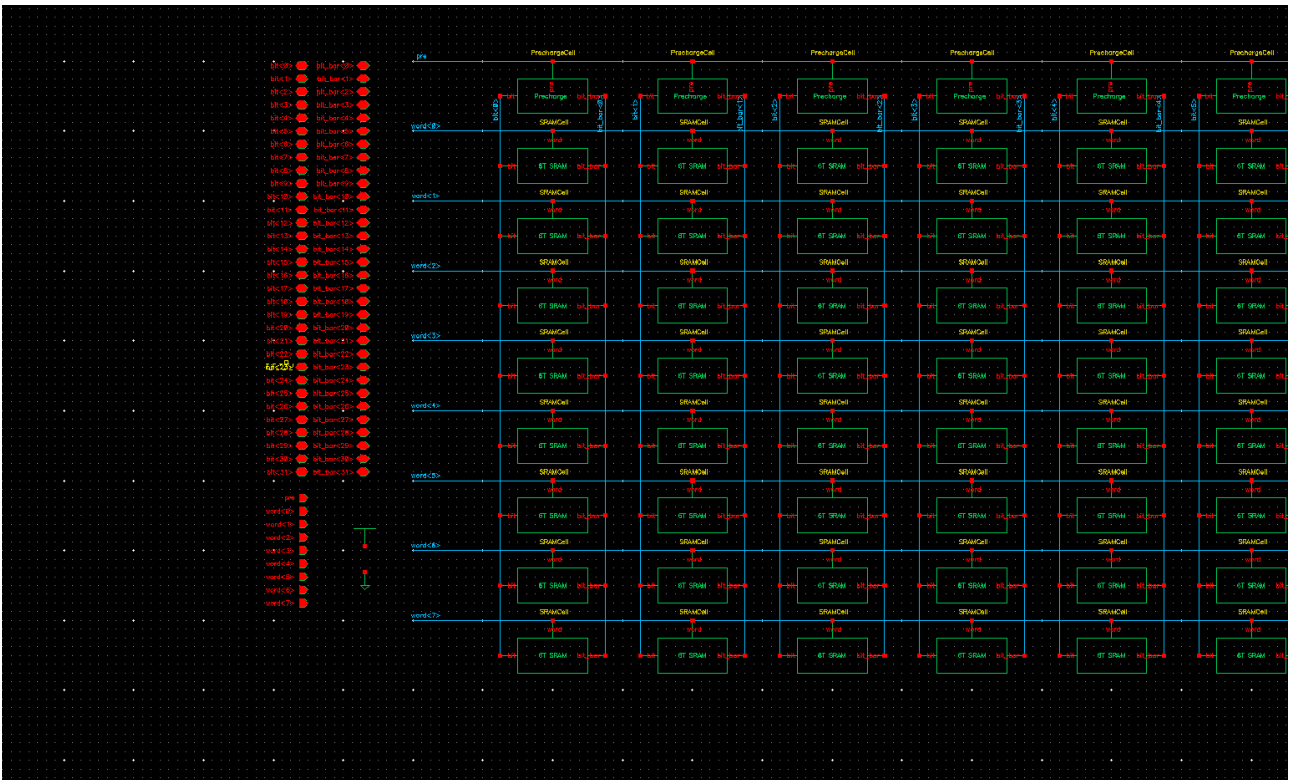
Each 256-bit SRAM bank was constructed with 8 row, 32 columns. The pre-charge was placed at the first row and connected to all the bit line and bit line bars.



SRAM 8x32 Bank (Layout)

 

The first row is the pre-charge system and following with 8 SRAM Cells.

 

PVS 16.15-64b Reports: Done [DRC] DR...

[LVS] LVS x [DRC] DRC x

```

ERC: Cumulative Time CPU = 0 (s) REAL = 0 (s)
PATTERN_MATCH: Cumulative Time CPU = 0 (s) REAL = 0 (s)
DFM FILL: Cumulative Time CPU = 0 (s) REAL = 0 (s)

Total CPU Time : 1 (s)
Total Real Time : 2 (s)
Peak Memory Used : 30 (M)
Total Original Geometry : 754 (56499)
Total DRC RuleChecks : 562
Total DRC Results : 0 (0)
Summary can be found in file SRAM_Bank_8x32.sum
ASCII report database: /home/viterbi/01/tchueh/work_gpdk045/DRC/SRAM_Bank_8x32
Checking

```

Design Rule

Lab1::SRAM_Bank_8x32::layout

Cell/Rule Hier Top Cells Rules Show:

Explain Return On Top

Cell/Rule	Color	Count	Level
Total: 0 results in 0 of 562 checks. Total number of non-empty checks is 0.			

Find

Error List

Help

/home/viterbi/01/tchueh/work_gpdk045/DRC/SRAM_Bank_8x32

PVS 16.15-64b Reports: Done [LVS] LV...

[DRC] DRC x [LVS] LVS x

```

#####
#
# Run Result : MATCH #
#
# Run Summary : [INFO] ERC Results: Empty #
# : [INFO] Extraction Clean #
# : [INFO] Some Sections Have Been Truncated #
#
# ERC Summary File : SRAM_Bank_8x32.sum #
# Extraction Report File : SRAM_Bank_8x32.rep #
# Comparison Report File : SRAM_Bank_8x32.rep.cls #
#
#####

```

Checking in all SoftShare licenses.

PVS Comparison Finished. Thu Sep 23 22:06:20 2021

Find

Error List

Help

ReRun ReSubmit Close Report Kill

/home/viterbi/01/tchueh/work_gpdk045/LVS

PVS 16.15-64b LVS Run St...


ERC Results **Empty**

Extraction Results: **Clean**


Comparison Results: **Match**

Do you want to start the LVS DE? Yes No


SRAM 512-bit (Schematic)

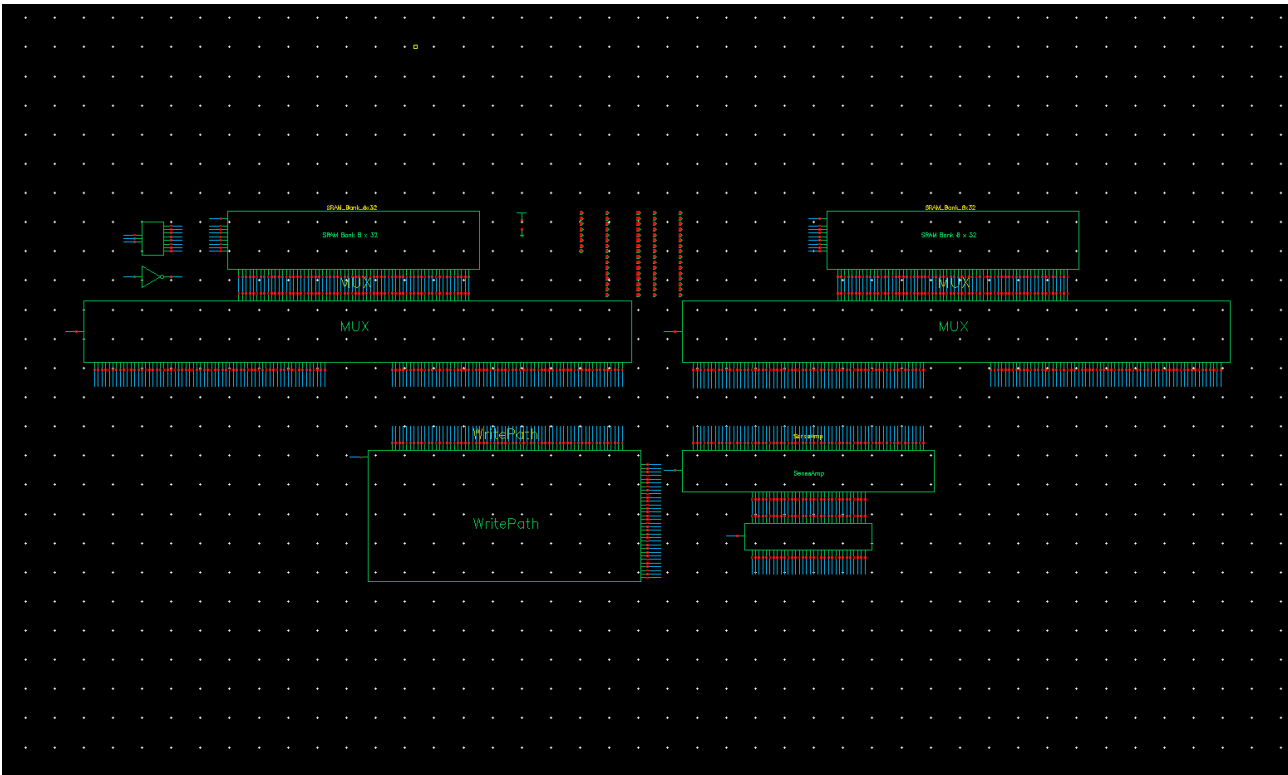

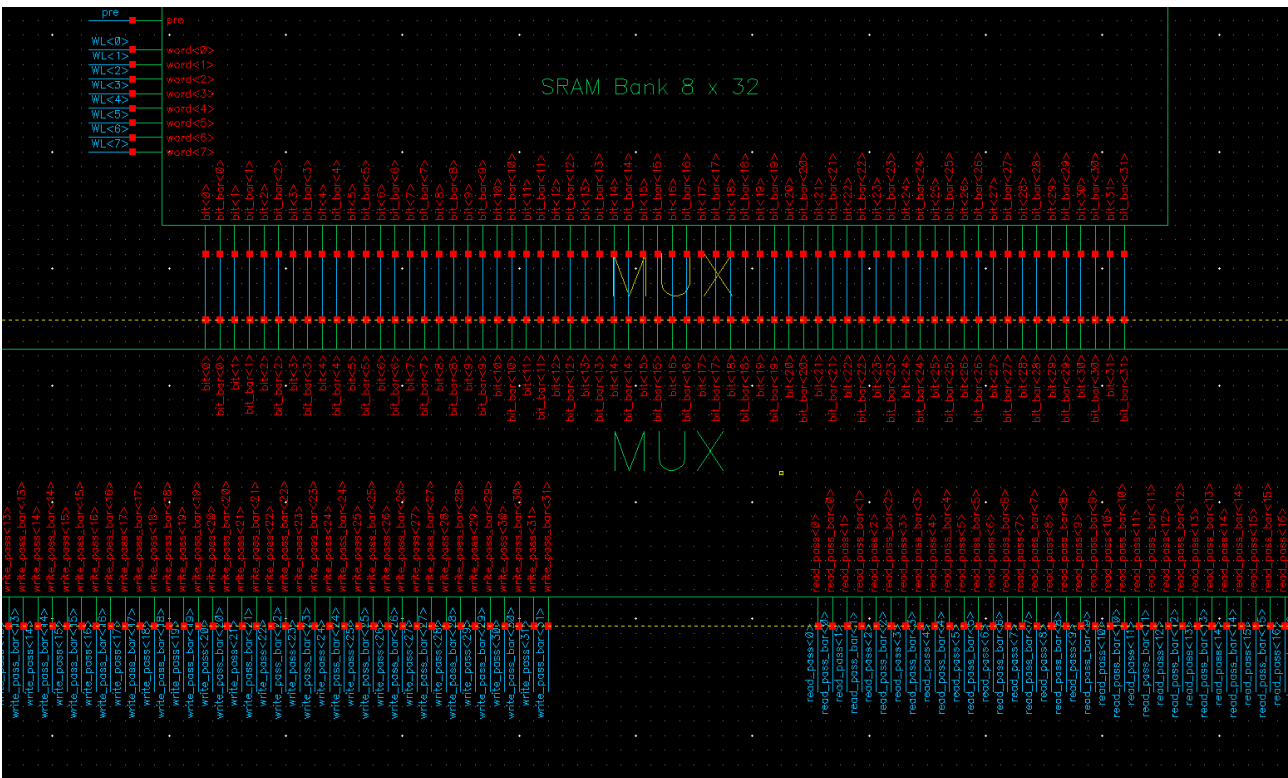
The SRAM Bank is connected to write/read MUX.



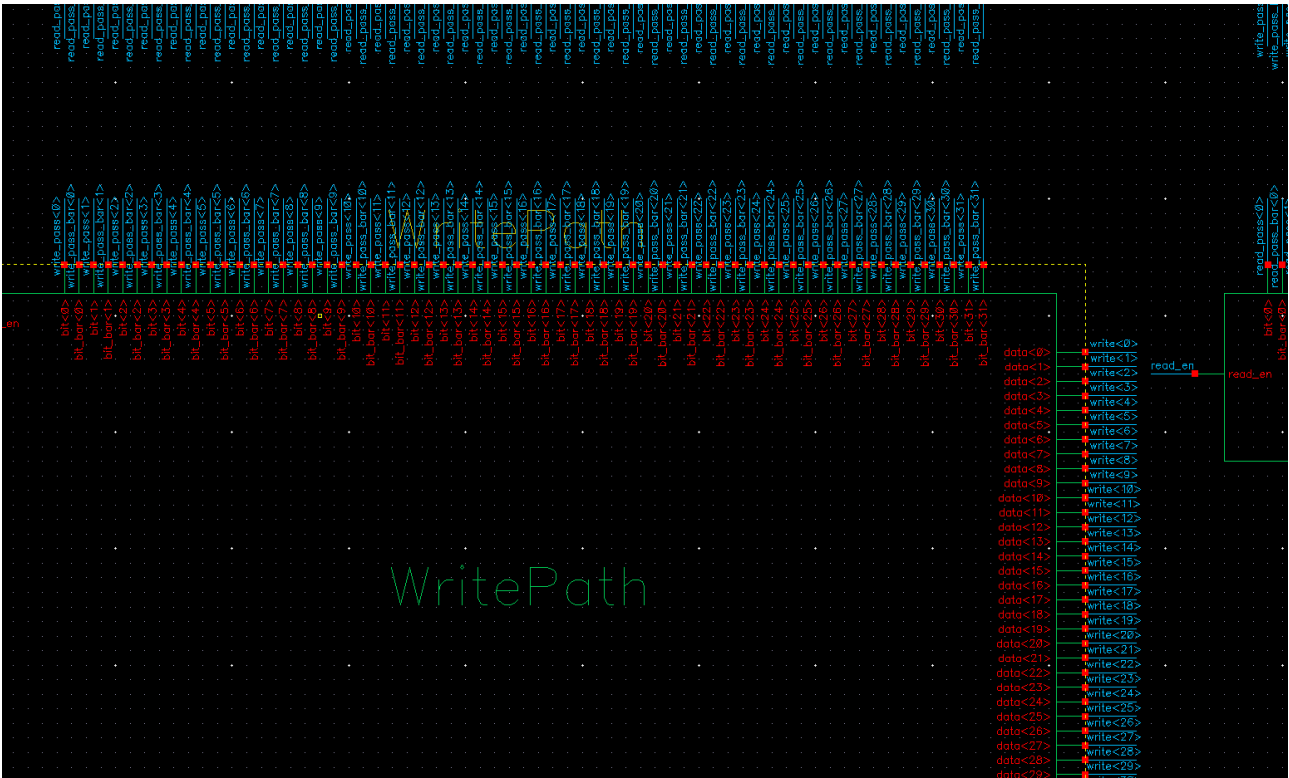
The write_pass of the MUX is connected to the bit line in Write Path.



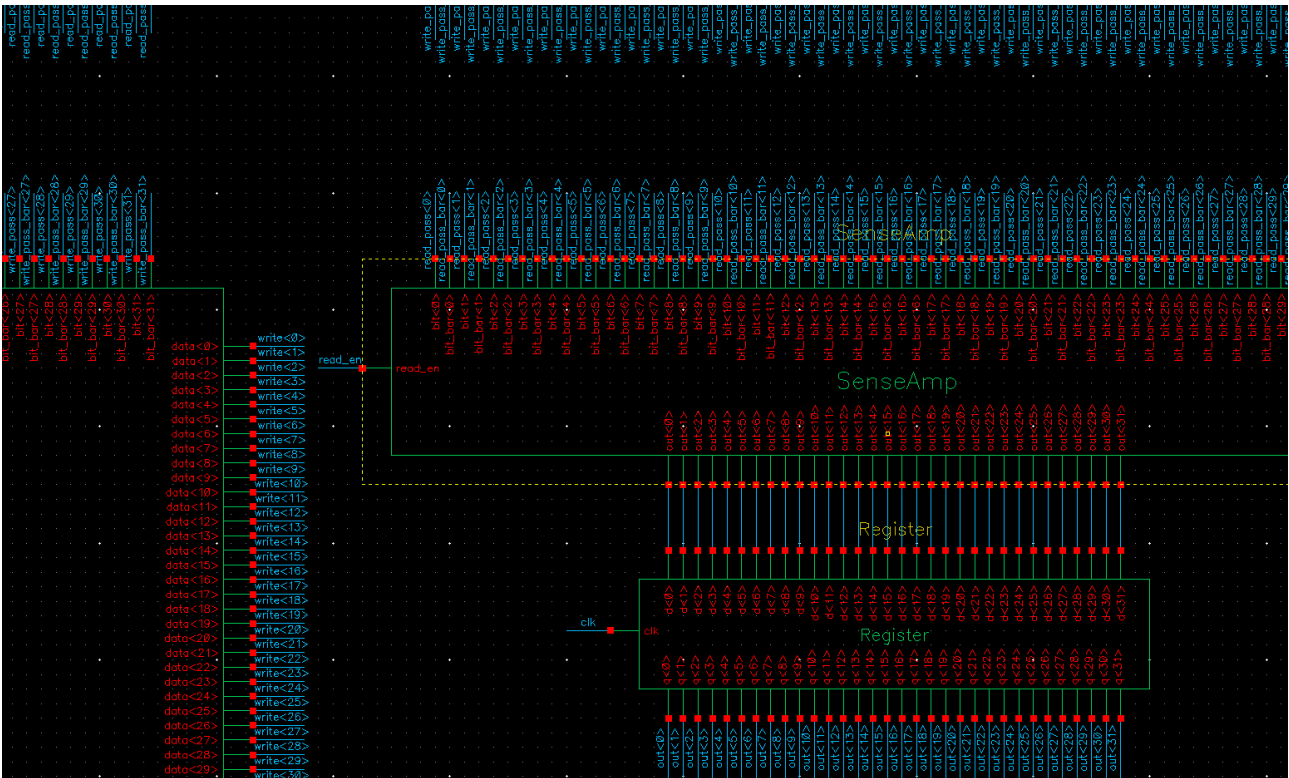
The read_pass of the MUX is connected to the bit line in Sense Amp.





The figure below is the I/O pins of the SRAM 512-bit.

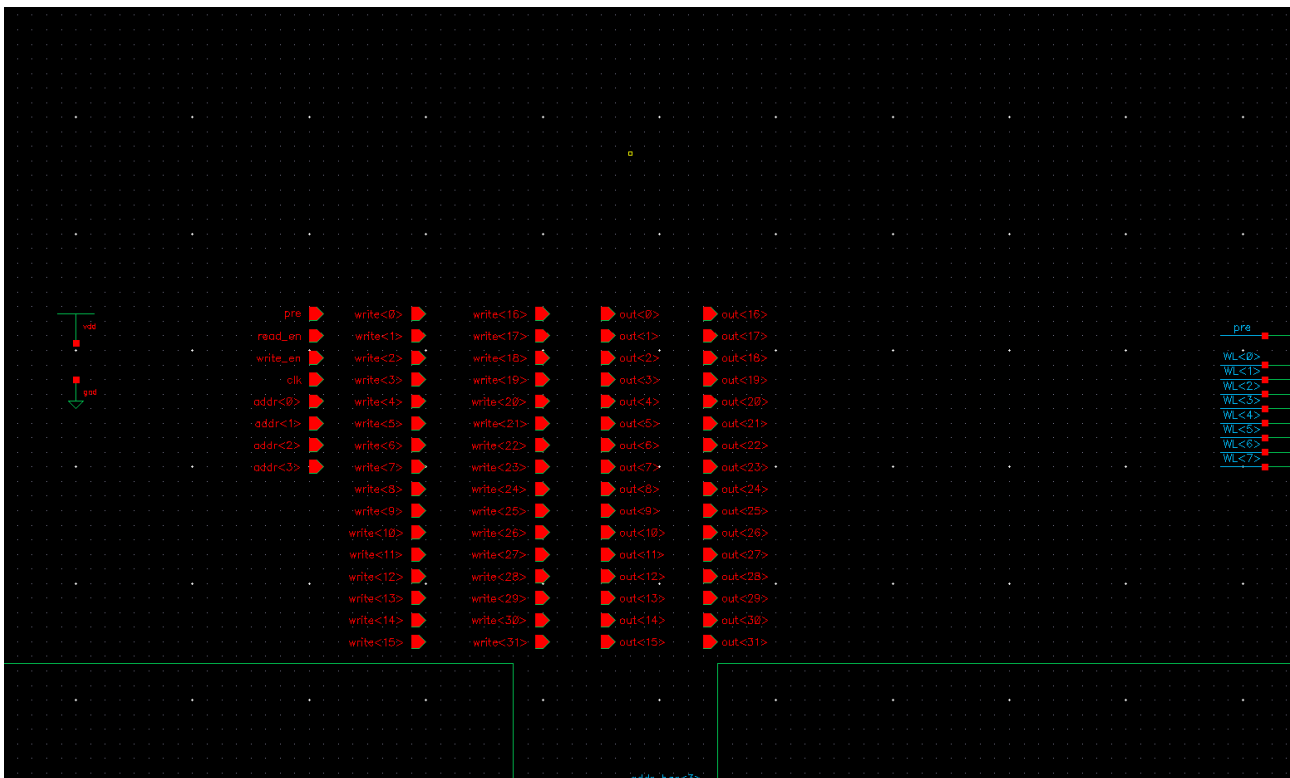


SRAM 512-bit (Layout)

 


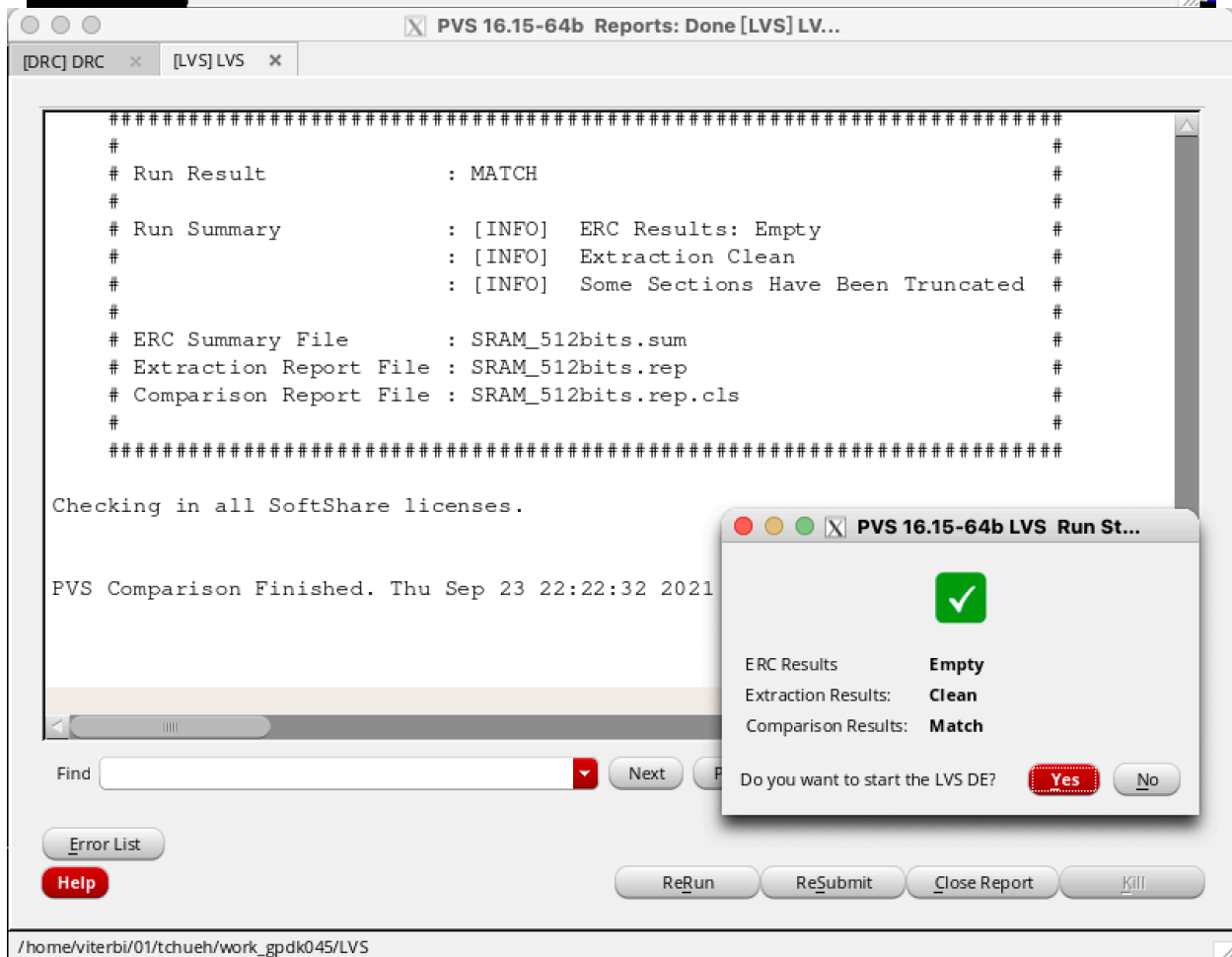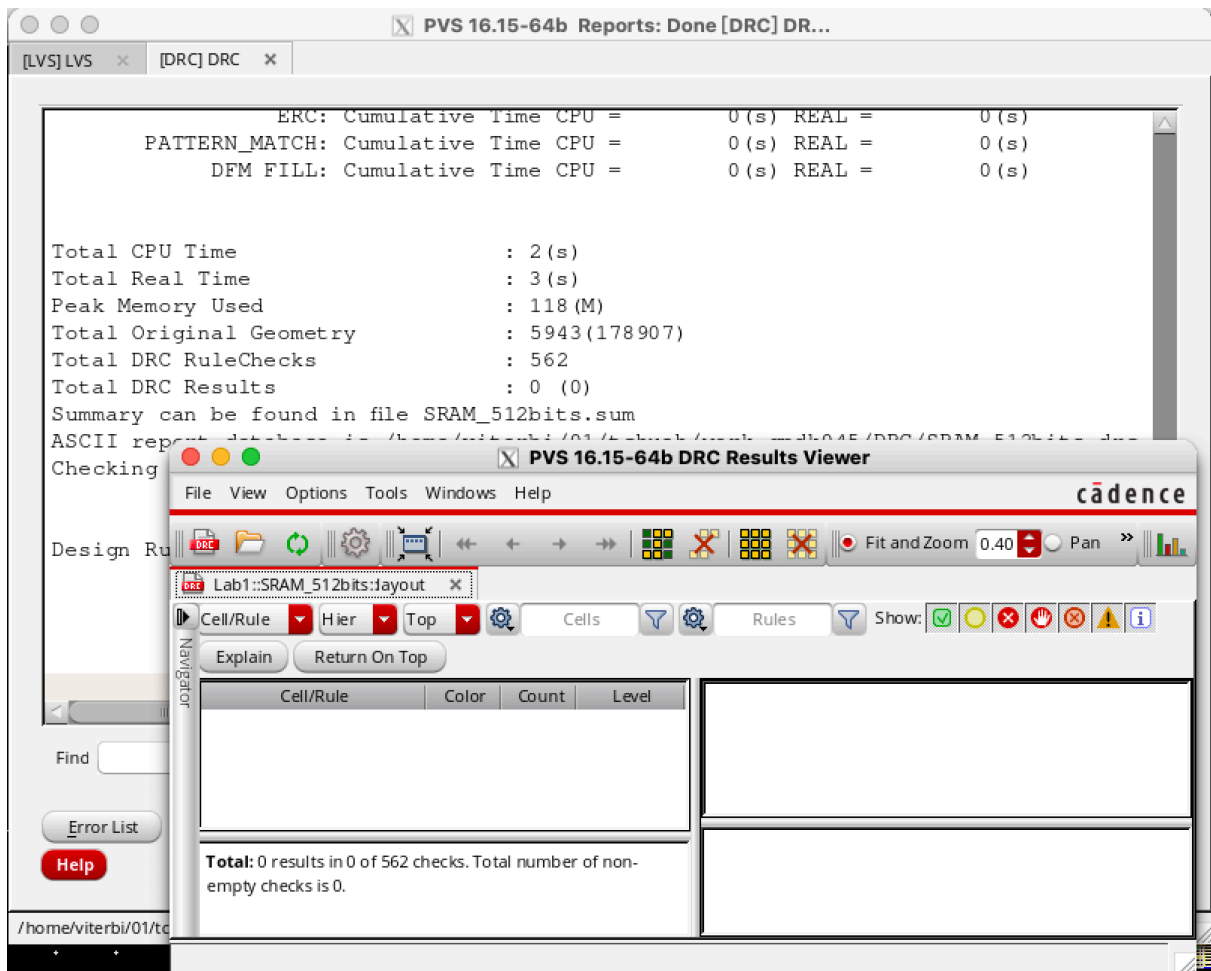


Read SNM is at least 190mV

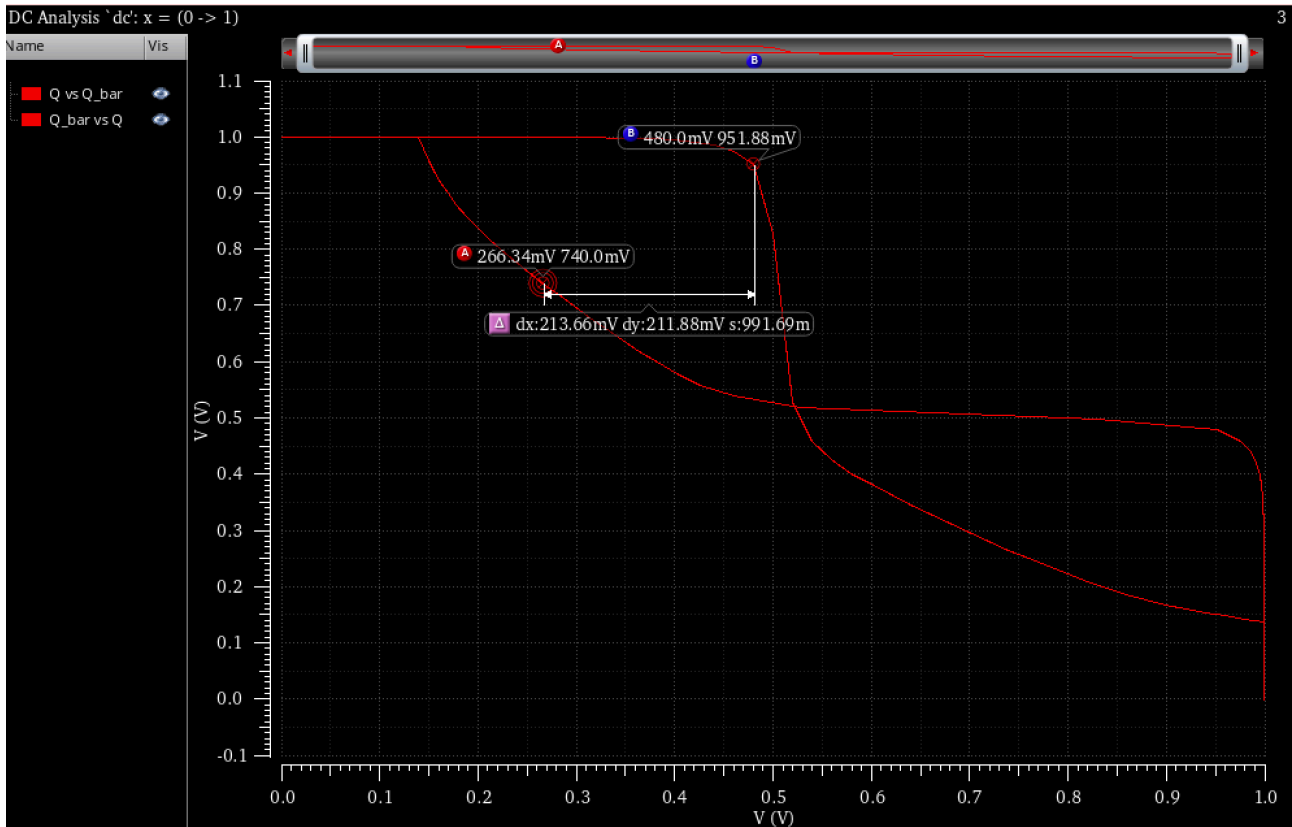

Write SNM is at least 395mV

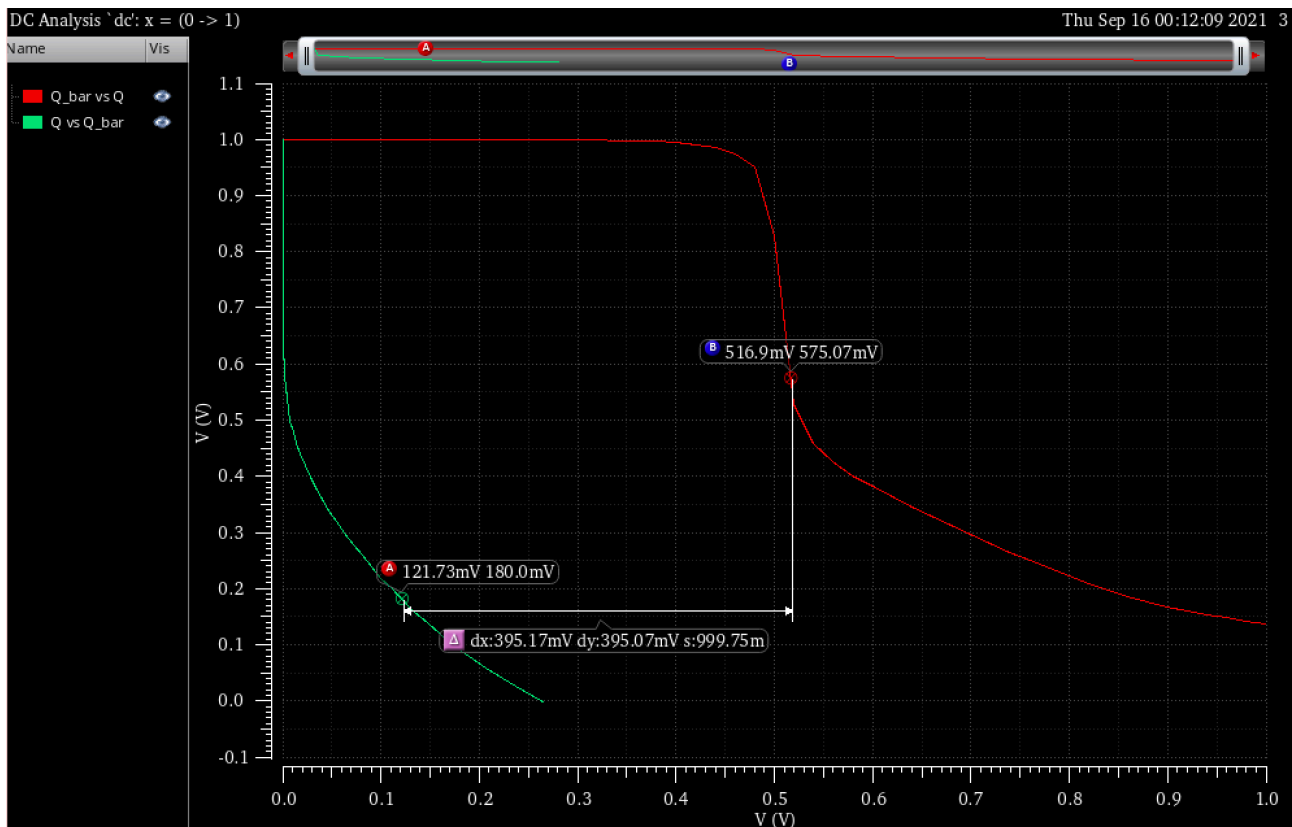

SRAM One Cell (Schematic)

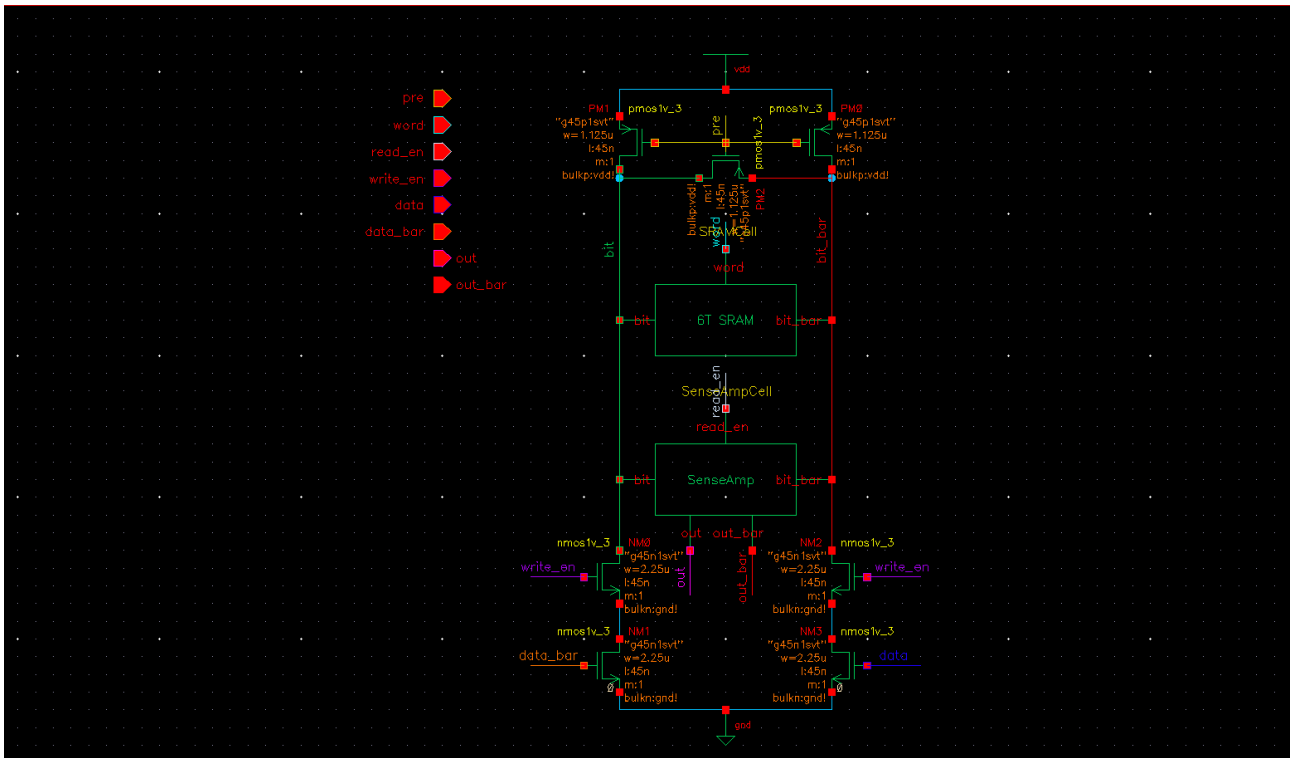

The figure below shows the simulation for the single SRAM Cell with the waveform of the operation Write 1 → Read → 1 → Write 0 → Read 0.



Write 1 Read 1 Write 0 Read 0
 12.57 ps 8.52 ps 11.49 ps 8.52 ps

SRAM operation:

During the write operation, the 32-bit input data will be send to the Write Path. The `addr<3>` is going decide which Memory Bank will save the data. After that, the output of the Write Path (bit / bit_bar) is pass through the nMOS pass transistors in the MUX and stored in the 256-bit SRAM Bank.

During the read operation, the address we got will decide which word line and which Memory Bank to read from. The Sense Amplifier sense the difference in the bit and bit_bar when the pMOS pass transistors in the MUX tuns on.

Register at the output controls the information when it is available at the clock edge as the Sense Amplifier sense the difference.

Summary:

Area $173.325 \times 38.807 = 6726.22328 \mu\text{m}^2$



Complete time: 160 ns



Clock Frequency: $1/4 \text{ ns} = 250 \text{ MHz}$

Read 10 data values (32 bit each) from a vector file and write into the SRAM in a sequential order starting from the last digit of your USC ID and then read 10 of them in the sequence of your USC ID.

SEQUENCE	A[3]-A[0]	DATA[31]-[0]
0	0100	143B B432
1	0101	2134 5321
2	0111	ABCD 1234
3	0110	2231 CCCC
4	0001	3211 7686
5	0010	ABCD 1111
6	1000	12AB CD91
7	1001	1296 CD21
8	1010	7A5A 6531
9	1100	6432 851A

SRAM 512-bit (Schematic Waveform)

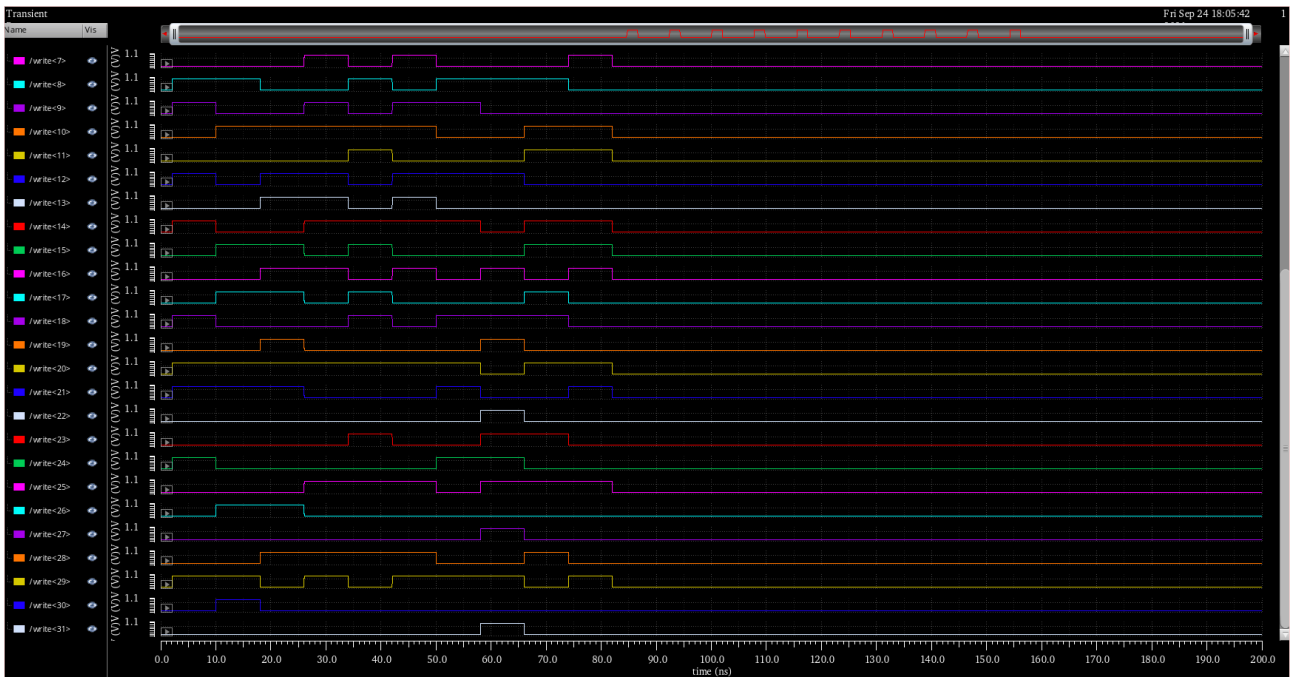 

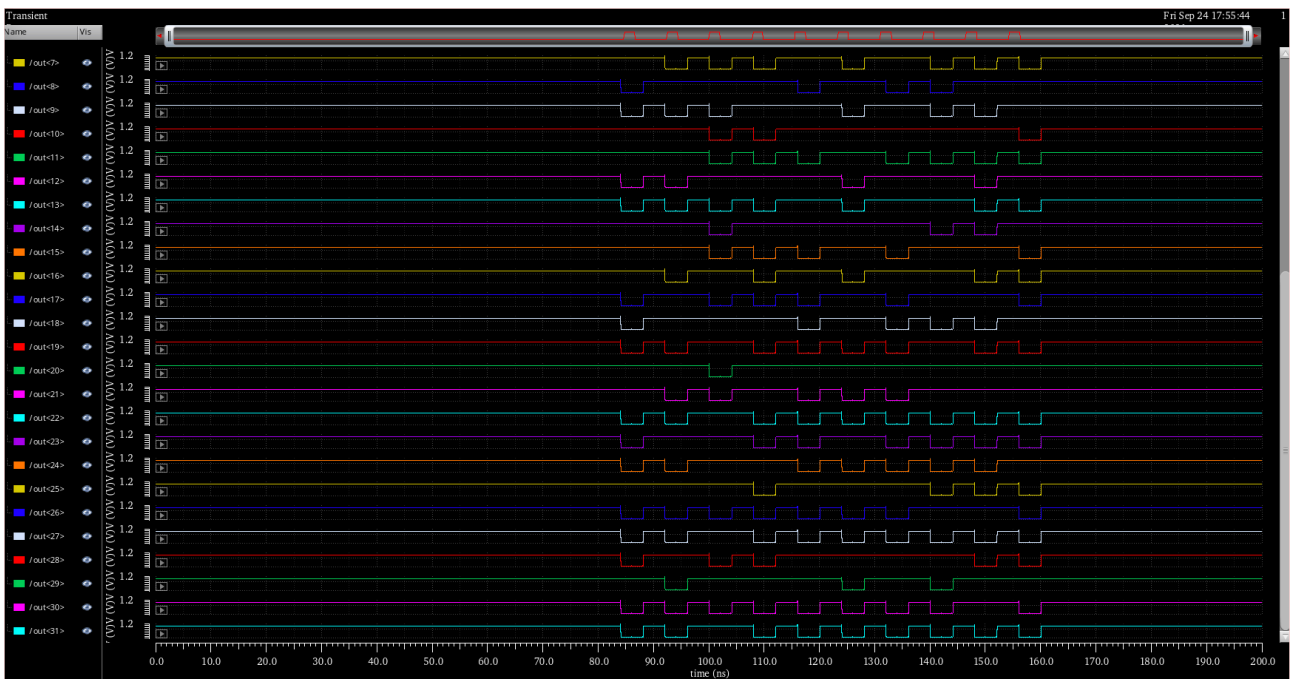 

SRAM 512-bit (Extracted Waveform)

